



SWINBURNE
UNIVERSITY OF
TECHNOLOGY

COS10004 Computer Systems


Lecture 2.2 – Clocks (and introducing the ALU)

CRICOS provider 00111D

Dr Chris McCarthy

GATES ARE NOT INSTANTANEOUS

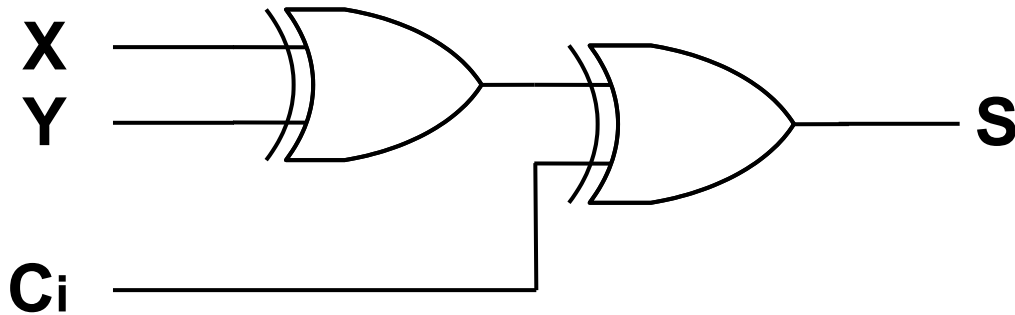
Changing the state of a gate takes some finite time.



What's the issue here ?

GATES ARE NOT INSTANTANEOUS

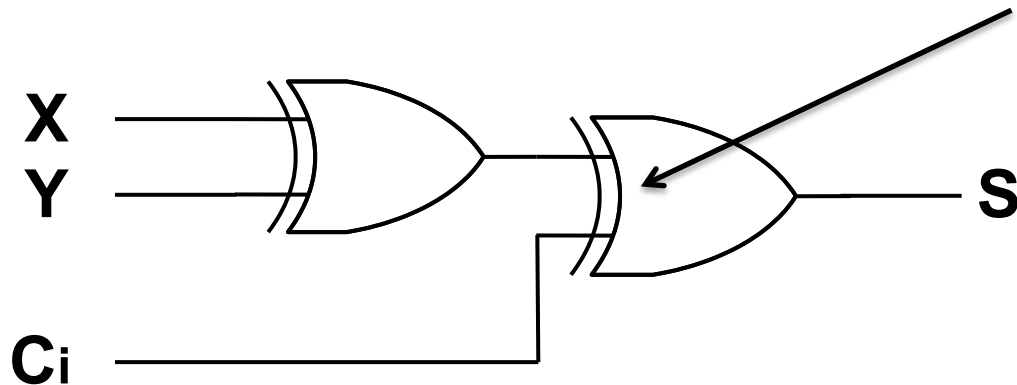Changing the state of a gate takes some finite time.



Ci and the output of X XOR Y will arrive at different times!!!


The circuit is **unstable**.

If only we could synchronise things !!

What's the issue here ?

GATES ARE NOT INSTANTANEOUS

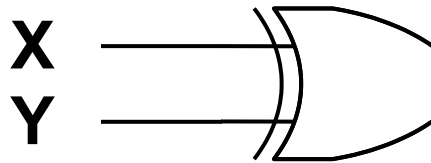Changing the state of a gate takes some finite time.



Ci _____

What's the issue here?



The output of $X \text{ XOR } Y$ will
be different times!!!

The circuit is **unstable**.

We could synchronise

Clock

Could be something simple like a 555 timer (astable multivibrator using an RC timing element), a crystal oscillator, a phase-locked loop or an atomic clock. Probably just a chip.



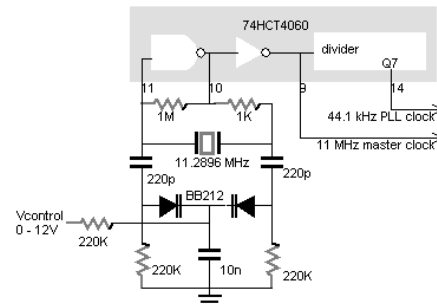
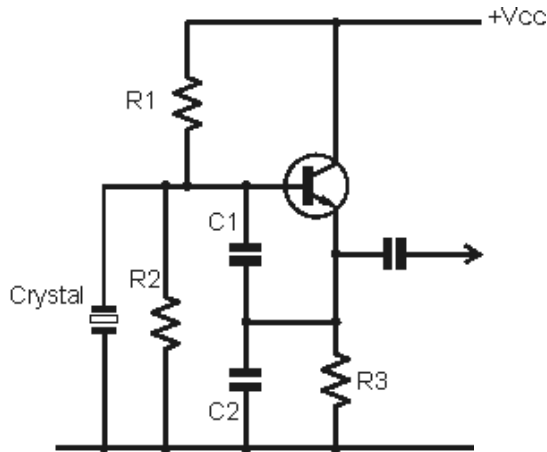
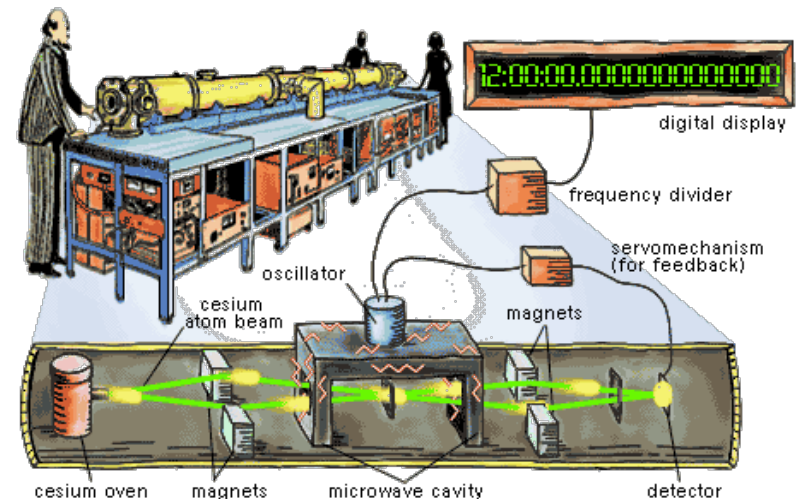


figure 7 Voltage Controlled Crystal Oscillator

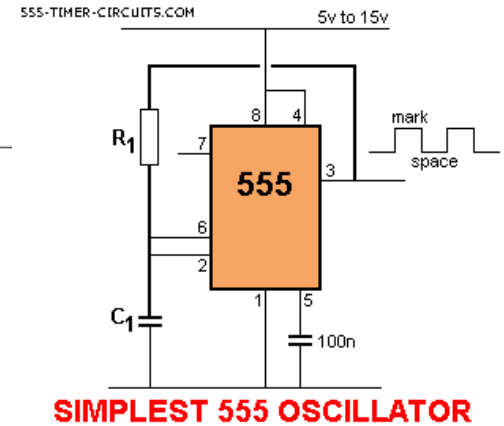


Clock feeds into the ALU

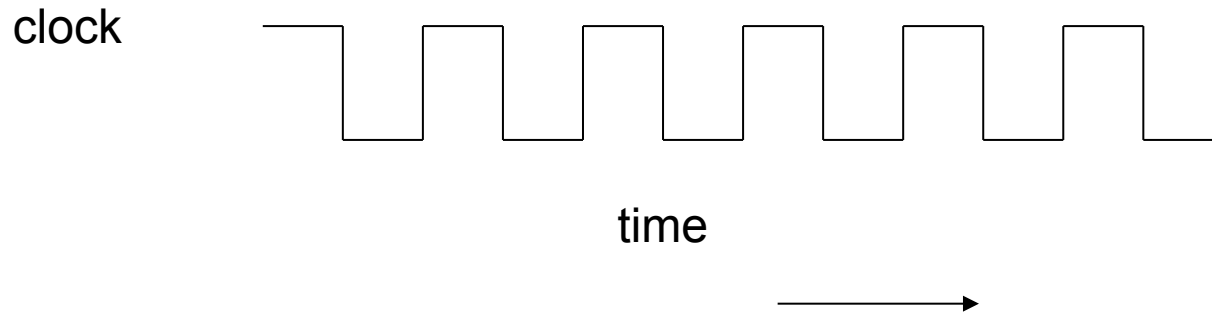



The *clock* is needed because bits need to “settle” before you can use them.

Computers often have different clocks controlling different parts.

Clock feeds into the ALU

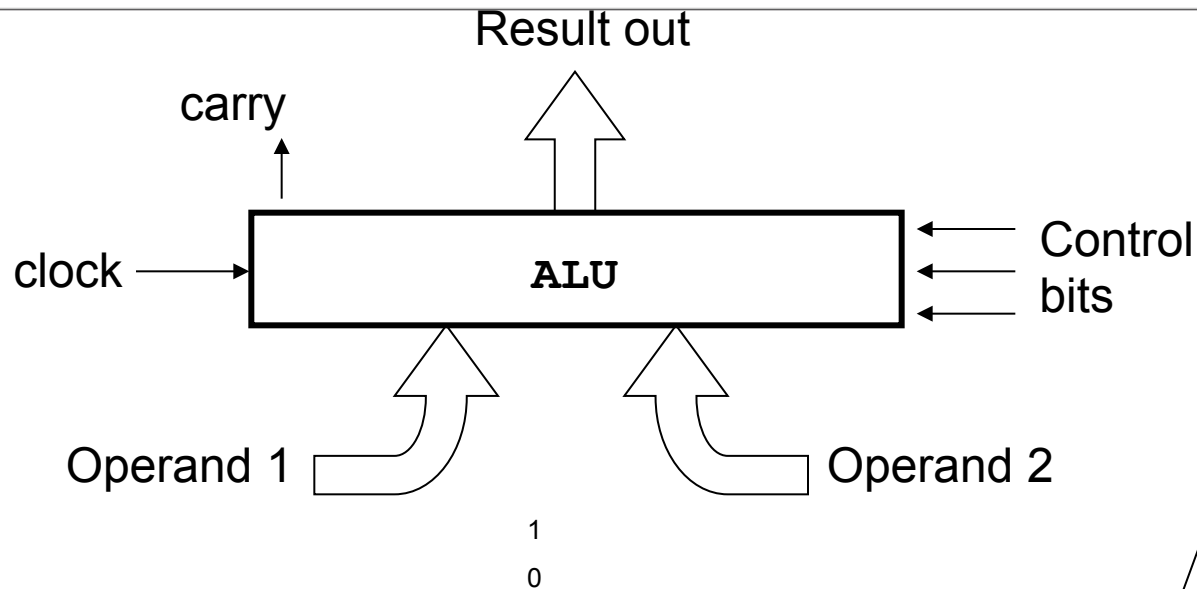

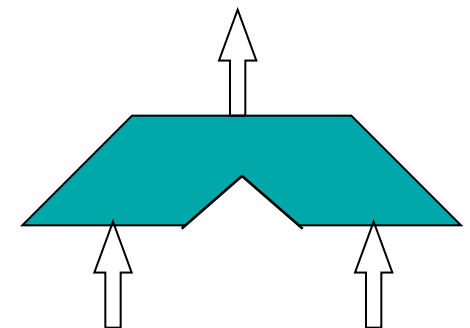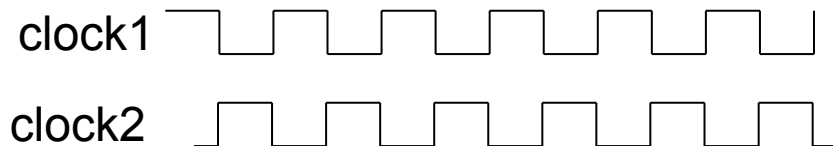Often an ALU needs 2 clock bits *out of phase*:



Common symbol
for ALU

Summary

- > Clocks ensure data flow is synchronised in a circuit:
 - Ensures predictability
 - Avoid illegal/ill-defined states
- > Arithmetic Logic Unit:
 - Where integer calculations and bit shifting operations are performed
- > We'll come back to both these topics!
- > Next Lecture: Storing bits